

## OHM'S LAW

$$V = IR$$

$$P = \frac{V^2}{R} = I^2 R$$

## SERIES

$$R_{\text{eq}} = R_1 + R_2 + \dots$$

CURRENT IS THE SAME

$$V_{\text{in}} = V_{\text{TOTAL}} = \frac{R_N}{R_1 + R_2 + \dots}$$

$$C_{\text{eq}} = \frac{1}{C_1 + C_2 + \dots}$$

$$L_{\text{eq}} = L_1 + L_2$$

## KIRCHHOFF'S LAWS

$$\text{KCL} \quad I_{\text{IN}} = I_{\text{OUT}}$$

$$\text{KVL} \quad V_{\text{GAINS}} = V_{\text{LOSSES}}$$

## POWER

$$P = \frac{V^2}{R} = I^2 R = VI$$

## PARALLEL

$$R_{\text{eq}} = \frac{1}{R_1 + \frac{1}{R_2} + \dots}$$

$$I_{\text{IN}} = I_{\text{TOTAL}} = \frac{V_{\text{IN}}}{R_1 + \frac{1}{R_2} + \dots}$$

VOLTAGE SAME THROUGH EACH RESISTOR.

$$C_{\text{eq}} = C_1 + C_2 + \dots$$

$$L_{\text{eq}} = \frac{1}{L_1 + \frac{1}{L_2} + \dots}$$

## NODAL ANALYSIS

1. LABEL A NODE AS GROUND [IDEALLY ON ONE SIDE OF A VOLTAGE SOURCE]. LABEL OTHER NODES AS  $a, b, \dots$

2. LABEL UNKNOWN NODE VOLTAGES AS  $V_a, V_b, \dots$ , AND LABEL THE CURRENT IN EACH RESISTOR AS  $I_1, I_2, \dots$

3. WRITE KIRCHHOFF'S CURRENT EQUATIONS FOR EACH UNKNOWN NODE

4. REPLACE CURRENTS IN YOUR KCL WITH EXPRESSIONS LIKE THIS:  $\frac{V_a - V_b}{R_1}$

5. SOLVE THE MULTIPLE EQUATIONS FOR THE MULTIPLE UNKNOWN VOLTAGES

## INDUCTORS

$$V_L = L \cdot \frac{di}{dt} i_L$$

$$i_L = \frac{1}{L} \int_0^t V_L dt + i_L(0)$$

SINUSOIDS

$$V_L(t) = \frac{L \omega_i I_p \sin(\omega t)}{V_p}$$

IF INDUCTOR HAS BEEN CONNECTED FOR A LONG TIME,  
THE INDUCTOR WILL LOOK LIKE A SHORT

$$i_L(t) = I_p \cos(\omega t)$$

## CAPACITORS

$$i_C = C \cdot \frac{dv}{dt} v_C$$


$$v_C(t) = \frac{1}{C} \int_0^t i_C dt + v_C(0)$$

SINUSOIDS

$$V_C(t) = \frac{1}{C} \frac{1}{\omega} I_p \sin(\omega t) \quad i_C(t) = I_p \cdot \cos(\omega t)$$


IF CAPACITOR HAS BEEN CHARGING FOR A LONG TIME,  
THE CAPACITOR WILL LOOK LIKE AN OPEN

## CAPACITOR + INDUCTOR IN SERIES

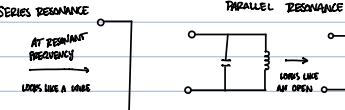

RESONANT FREQUENCY:
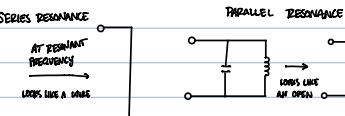
$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{OR} \quad \omega_0 = \frac{1}{\sqrt{L/C_0}}$$



## FIRST ORDER TRANSIENT CIRCUITS

FOR ALL FIRST ORDER TRANSIENTS

$$V_x(t) = V_x(\infty) + (V_x(0) - V_x(\infty)) e^{-\frac{t}{\tau}}$$

$$i_x(t) = i_x(\infty) + (i_x(0) - i_x(\infty)) e^{-\frac{t}{\tau}}$$

$$\text{RC IN SERIES} \quad \gamma = R_m C \quad \text{WHEN } R_m \rightarrow \infty$$

$$\text{RL IN SERIES} \quad \gamma = \frac{L}{R_m} \quad \text{WHEN } L \rightarrow \infty$$

## AC

VOLTAGES THAT CHANGE WITH TIME

$$V(t) = V_p \cos(\omega t + \phi)$$

$$i(t) = I_p \cos(\omega t + \phi)$$

$$f = \frac{1}{T}$$

$$\omega = 2\pi f$$

$$\phi = \frac{-\omega t}{T} - 360^\circ = \frac{-\omega t}{T} \cdot 2\pi$$

$$\text{CONVERSION} \quad a + bi = \left( \sqrt{a^2 + b^2} \right) e^{j \arctan(\frac{b}{a})}$$

$$e^{j\alpha} = \cos(\alpha) + j\sin(\alpha) \quad \cos(\alpha) = \frac{e^{j\alpha} + e^{-j\alpha}}{2}$$

$$e^{j(\omega t + \theta)} = \cos(\omega t + \theta) + j\sin(\omega t + \theta) \quad \sin(\alpha) = \frac{e^{j\alpha} - e^{-j\alpha}}{2j}$$

## RECTANGULAR

$$A \cdot D = (a + bi)(c + di) = (ac - bd) - (bc - ad)i$$

$$\frac{A}{D} = \frac{a + bi}{c + di} = \frac{ac + bd}{c^2 + d^2} + \frac{bc - ad}{c^2 + d^2} i$$

## POLAR

$$A \cdot D = A e^{j\theta} D e^{j\phi} = AD e^{j(\theta + \phi)}$$

$$\frac{A}{D} = \frac{A e^{j\theta}}{D e^{j\phi}} = \frac{A}{D} e^{j(\theta - \phi)}$$

## IMPEDANCE

$$Z_i = j\omega L \quad Z_o = \frac{-j}{\omega C} \quad Z_p = R$$

USED FOR ADDING & SUBTRACTING SHARDED WAVEFORMS

PHASOR  
 $V(\omega) = V_p \cdot e^{j\phi}$  } Frequency Domain  
 $I(\omega) = I_p \cdot e^{j\phi}$

YOU CAN'T ADD VECTORS IN POLAR FORM

$$I_{Zn} = I_{\text{TOTAL}} \cdot \frac{\frac{1}{Z_n}}{\frac{1}{Z_1} + \frac{1}{Z_2} + \dots}$$

$$I_{\text{PHASOR}} = \frac{V_{\text{PHASOR}}}{Z_{eq}}$$

$$V_{Zn} = V_{\text{TOTAL}} \cdot \frac{Z_n}{Z_1 + Z_2 + \dots}$$

## FILTERS

A FILTER PASSES SOME FREQUENCIES & FILTERS OUT OTHER FREQUENCIES

HIGH PASS: PASSES HIGH FREQUENCIES, REJECTS LOW

LOW PASS: PASSES LOW FREQUENCIES, REJECTS HIGH

$\omega_c$  = CORNER FREQUENCY

## TRANSFER FUNCTION

$$H(s) = \frac{V_{\text{OUT}}}{V_{\text{IN}}} \quad \begin{matrix} \text{TOP} = 0 \rightarrow \text{ZERO} \\ \text{BOTTOM} = 0 \rightarrow \text{POLE} \end{matrix}$$

## 2ND ORDER TRANSIENTS

CHARACTERISTIC EQUATION ← BOTTOM PART OF CHARACTERISTIC EQUATION

$$s^2 + \underline{\quad} s + \underline{\quad} = 0$$

LAPLACE IMPEDANCES

INDUCTOR →  $Ls$

CAPACITOR →  $\frac{1}{Cs}$

RESISTOR →  $R$

$s_1, s_2$  REAL & NEGATIVE  
OVERDAMPED

$s_1, s_2$  EQUAL  
CRITICALLY

UNDERDAMPED

$$b^2 - 4ac > 0$$

$$b^2 - 4ac = 0$$

$$b^2 - 4ac < 0$$

$$V = V(\infty) + Be^{st} + De^{st}$$

$$V = V(\infty) + e^{\alpha t} (B\cos(\omega t) + D\sin(\omega t))$$

$$s = \alpha + j\omega$$

$$\natural \text{ NATURAL FREQUENCY} = \omega_n = \sqrt{\alpha^2 - \omega^2}$$

### TO SOLVE:

- DRAW FINAL CONDITIONS: FIND  $v(\infty)$  OR  $i(\infty)$

- INITIAL CONDITIONS: FIND  $i(0)$  &  $v(0)$

- DRAW  $i(0)$  (BEFORE SWITCH TRNS)

- DRAW  $v(0)$  (AFTER SWITCH TRNS)

-  $i_L$  AND  $v_C$  CANNOT CHANGE INSTANTLY  
SO MODEL INDUCERS & CURRENTS AS  
CURRENT & VOLTAGE SOURCES

### SLOPE OF INITIAL CONDITIONS

$$\frac{di_L}{dt} = v_L \quad \frac{dv_C}{dt} = i_C$$

- USE INITIAL CONDITIONS AND/OR INITIAL SLOPES TO  
SOLVE TRANSIENT EQUATION

## SYSTEMS

$$X_{in}(s) \xrightarrow{H(s)} X_{out}(s) = X_{in}(s) \cdot H(s)$$

## DIODES



## REVIEW

SATURDAY {  
 - THESE  
 - BODE PLOTS  
 - DIODES

MONDAY {  
 - 2ND ORDER TRANSISTORS ~ P  
 - TRANSFER FUNCTION P  
 - DAMPING P  
 - FILTERS P

MAYBE:  
 - PHASORS

WILL MOST  
LIKELY BE ON  
EXAM

## EXAM MATERIAL

- BODE PLOT  
 - 2ND ORDER TRANSIENTS  
 -  $H(s)$  FROM A CIRCUIT

USUALLY ON FINAL

CHARACTERISTIC EQUATION

INITIAL & FINAL CONDITIONS

FIND  $i_c(t)$  OR  $v_c(t)$

SYSTEMS

10-20%  
POSSIBILITY

• FEEDBACK SYSTEMS  
• DIODE DC PROBLEM

• NOTE: AC POWER + RMS IS NOT ON  
THIS EXAM. THEY WILL BE LATER IN  
CLASS

DO 2 OR 3 PRACTICE TESTS IN PREP  
FOR REVIEW SESSIONS